

# Transistors

# Semiconductors

Impurities in the semiconductor material makes it a wonder material also called doping

*n*-type, donor - electrons as a majority carrier

*p*-type, acceptor - holes as a majority carrier

# Diodes

Combination of two material  $p$ -type and  $n$ -type

Forward biased - like a conductor, majority carrier is the conductor, low resistance


Reverse biased - like a very high resistance, minority carrier is the conductor

Works as a one-way flow control

# Transistors

- It's a three layer (terminal) semiconductor device
- Two  $n$  and one  $p$  type or two  $p$  and one  $n$  type layers
- Two  $n$  and one  $p$  type is *npn transistor*
- Two  $p$  and one  $n$  type is *pnp transistor*
  
- *Two types-*
  - *Bipolar junction transistor(BJT)*  
Both electrons and holes participate in current flow
  - *Unipolar junction transistor(UJT)*  
Only one, either electrons or holes participate in current flow




# Transistor family

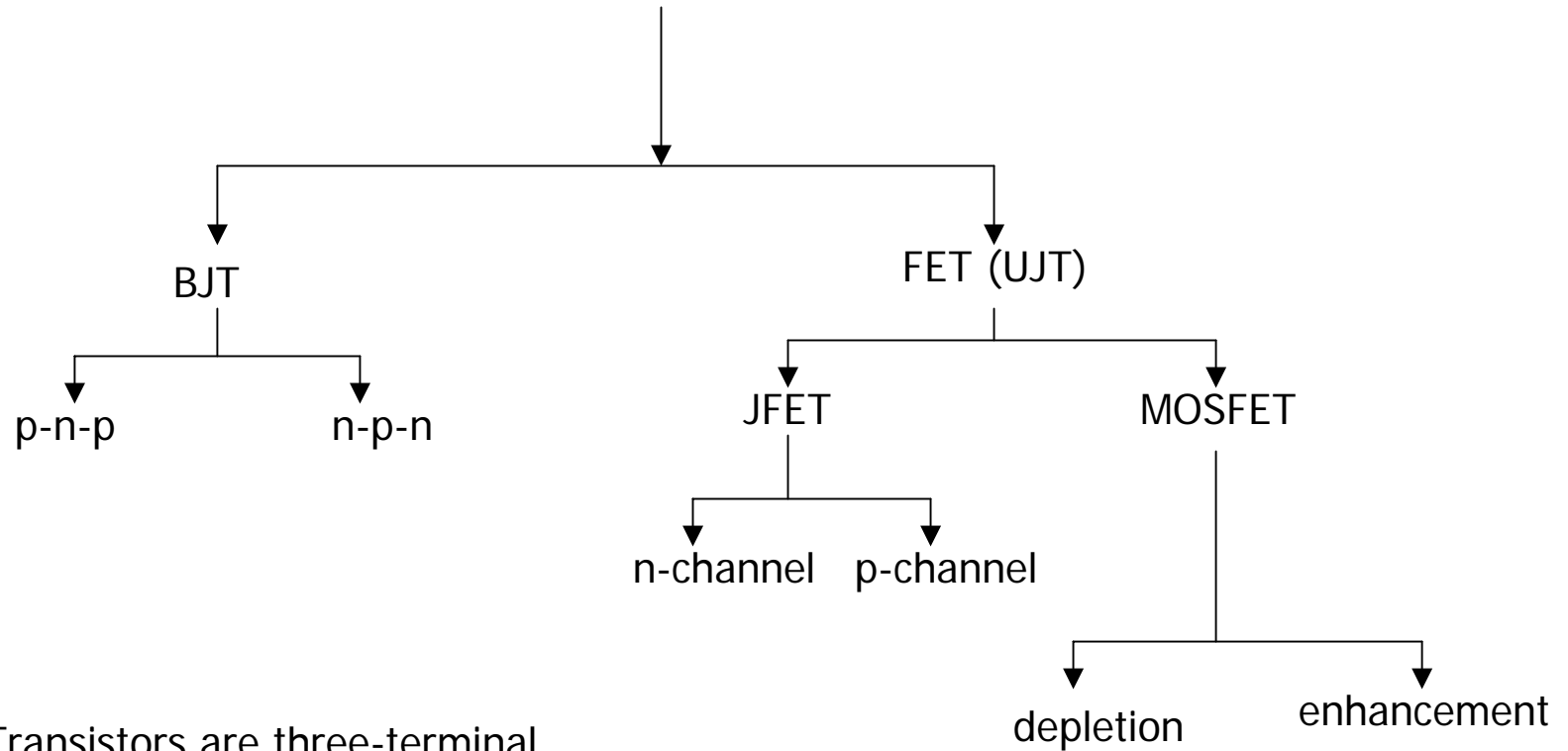


Transistors are three-terminal semiconductor devices
   
# Transistors

- Three terminals - Emitter, base, collector
- Middle layer or sandwich layer
  - thin compare to outer layers
  - lightly doped, less free carriers
- Can be considered as two diodes connected back to back



(a)

 


(b)

# Transistor operation

Forward biased diode -  $pn$  junction, emitter-base

Base- collector is open circuit.

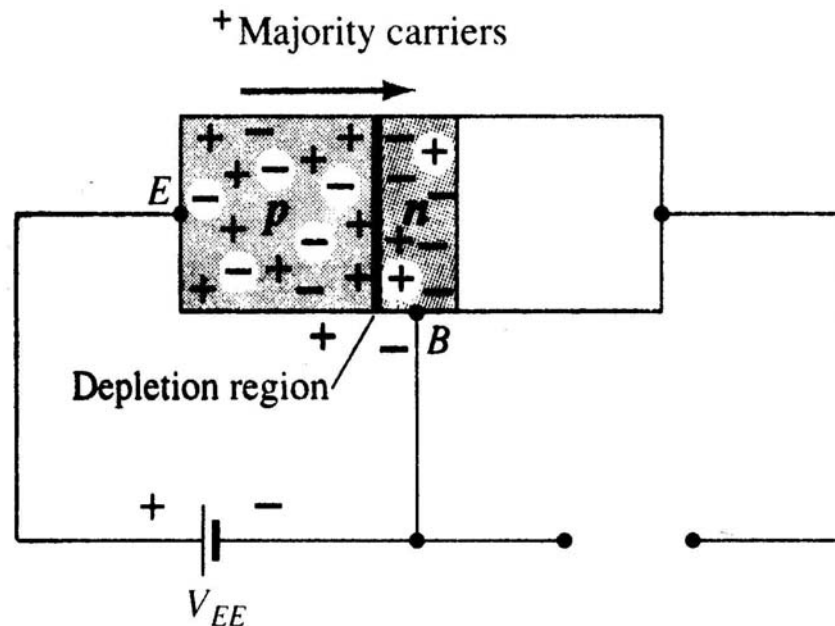Depletion layer is reduced and behave like a normal diode




Forward biased junction of a  $pnp$  transistor
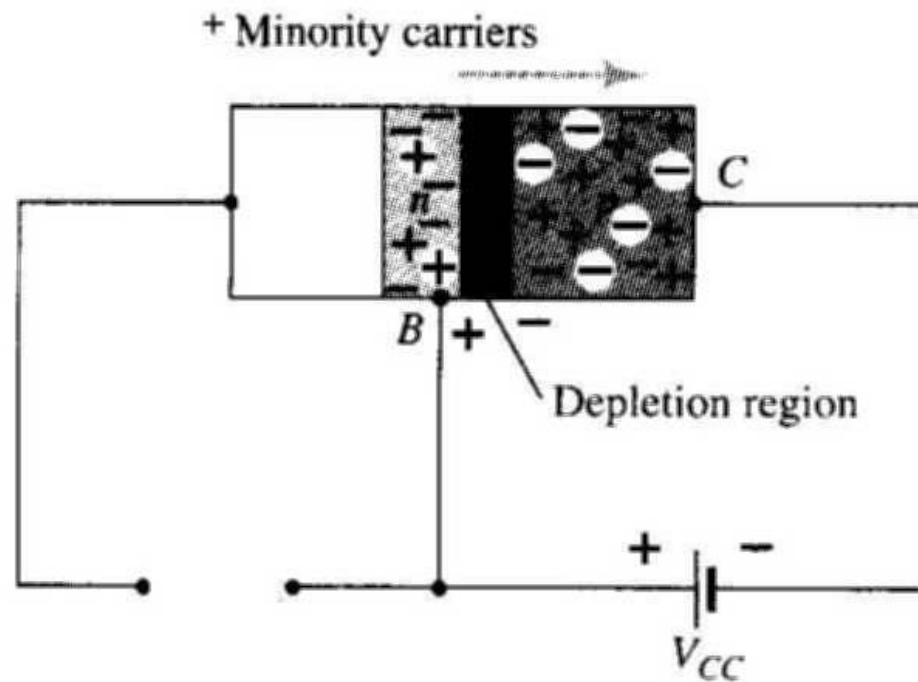
# Transistor operation

Reverse biased diode -  $np$  junction, base collector

Depletion layer is increased and behave like a reverse biased diode





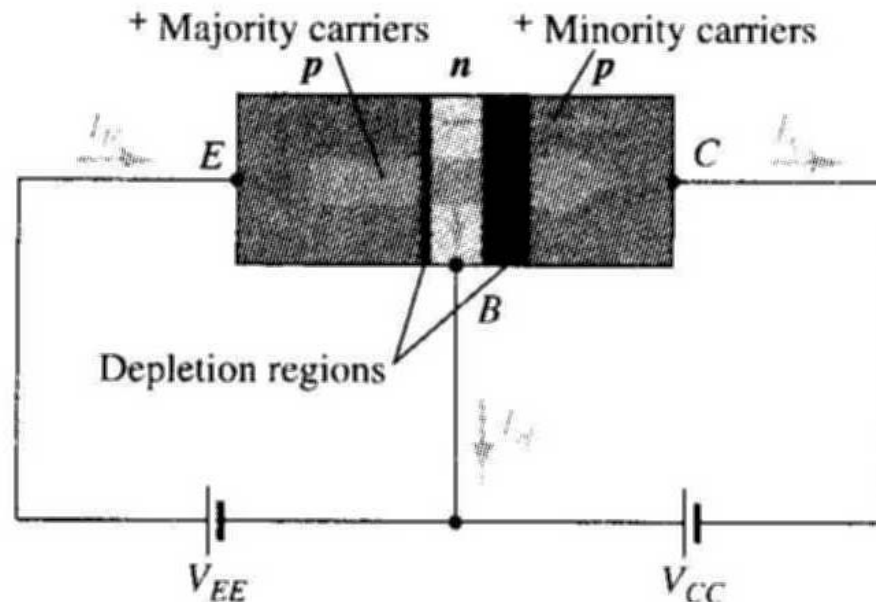
# Transistor operation

Forward biased emitter-base, and reverse biased base collector

Base is lightly doped, unable to handle large majority carriers. Diffuse to collector which is reverse bias, ready to accept the diffused holes.



# Modes of transistor operation

- Common - base
- Common - emitter
- Common - collector

Particular terminal is common to both input and output


# BJT Transistors

The arrow on the emitter lead shows the direction of current flow, when emitter-base junction is forward biased, it is always from  $p$  to  $n$


Currents are positive when flows inside the transistors

For a  $pn$ p transistor it will be inward and for  $np$ n transistor it will be outward

# Common - base

 

*pnp* transistor

 

*npn* transistor

Current direction changes in the above two configuration


# Common - base

Base is common to input and output

Emitter-base junction is forward biased

Collector-base junction is reverse biased

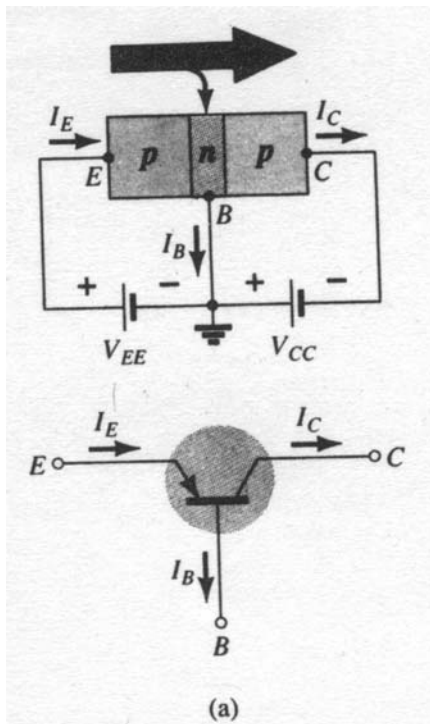
Biasing remains same irrespective of *npn* or *pnp*



Input characteristics  
for a common base  
silicon transistor


-like a *pn* junction

 -  $V_{CB}$  not having  
major influence


 
# Common - base

Active region - base-emitter forward biased and collector-base is reverse biased




# Common - base

$$I_E = I_B + I_C$$

Current in base is negligible.  
Current in emitter and collector is almost same.

Current gain less than unity
 
$$\alpha = I_C/I_E \quad (0.90 - 0.998)$$




# Common - emitter

Emitter is common to input and output

Base-emitter junction is forward biased

Collector-emitter junction is reverse biased

 Biasing remains same irrespective of *npn* or *pnp*






# Common - emitter

Base-emitter *pn* junction,  
forward biased

Base current is in micro ampere

 $V_{CE}$  does not have major  
influence on  $I_B$



(b)


# Common - emitter

Base-emitter  $pn$  junction,  
forward biased & base collector  
is reverse biased.

Base current is in micro ampere,  
collector current in milli ampere

High current gain

Cutoff region below  $I_B = 0$

 

(a)

# Common - emitter

$$I_C = \alpha I_E + I_{CBO}$$

$I_{CBO}$  current collector to base when emitter is open, minority current


$$I_E = I_B + I_C$$

$$I_C = \alpha (I_B + I_C) + I_{CBO}$$

$$I_C = \frac{\alpha I_B}{1 - \alpha} + \frac{I_{CBO}}{1 - \alpha}$$

Current Gain  $\beta = I_C / I_B$

$$\beta = (50 - 250)$$

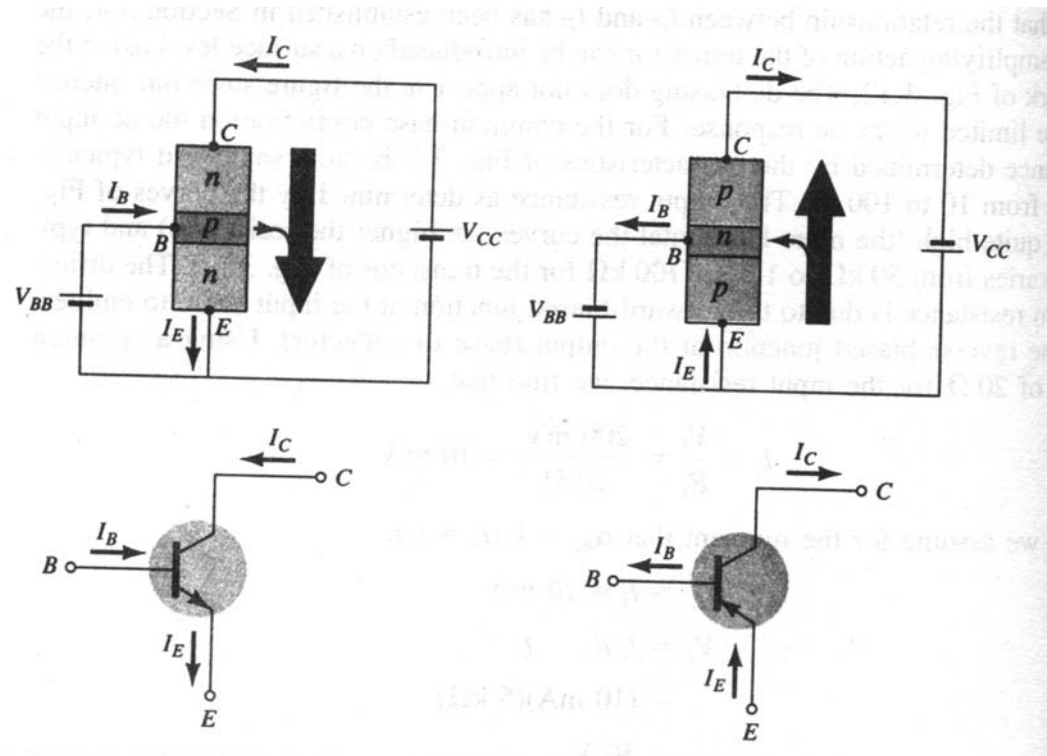

$$\beta = \frac{\alpha}{1 - \alpha}$$

$$\alpha = \frac{\beta}{1 + \beta}$$

# Common - collector

Collector is common to input and output


Base-collector junction is forward biased

Base-emitter junction is reverse biased

Biasing remains same irrespective of *npn* or *pnp*

Characteristics same as  
common emitter

 
Input resistance is very  
high and output resistance  
is low.


 
# DC Biasing - BJT

Biasing - shifting the mean operating point. To avoid operation in

- Non-linear region
- Saturation region
- Cut-off region
- Max. power consumption



Linear region operation

*Base-emitter forward bias*

*Base-collector reverse bias*

Cutoff region


*Base-emitter reverse bias*

Saturation region

*Base-emitter forward bias*


*Base-collector forward bias*

# DC Biasing - BJT

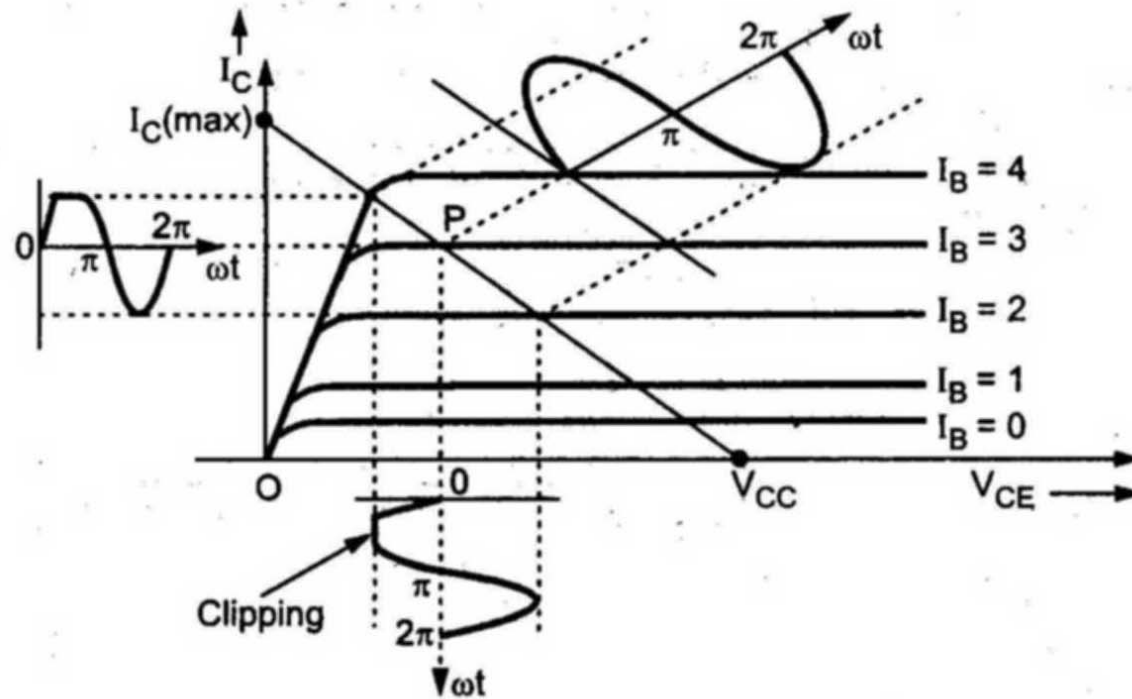


Clipping due to saturation region, base-collector junction gets forward biased

# DC Biasing - BJT

 

Clipping due to cutoff region.

# DC Biasing - BJT


 


Chosen Quiescent point is good for the given input signal



# Fixed Bias Circuit

Biasing is decided by the resistance  $R_B$  and  $R_C$  connected to base and collector. These decide the mean operating point. For DC analysis, circuit without capacitor can be analysed.

 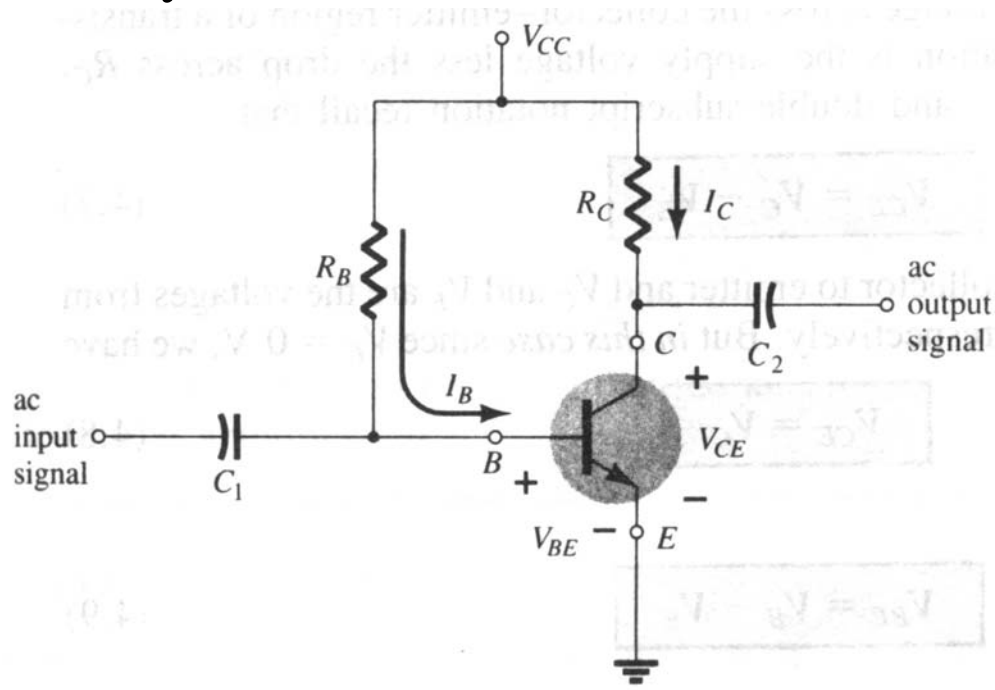

**Figure 4.3** Dc equivalent of Fig. 4.2.

# Fixed Bias Circuit

Base-emitter loop

$$+V_{CC} - I_B R_B - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

 


Figure 4.4 Base-emitter loop.

# Fixed Bias Circuit

Collector-emitter loop


$$I_C = \beta I_B$$

$$V_{CE} + I_C R_C - V_{CC} = 0$$

$$V_{CE} = V_{CC} - I_C R_C$$


$$V_{CE} = V_C - V_E$$

$$V_{BE} = V_B - V_E$$

 


**Figure 4.5** Collector-emitter loop.

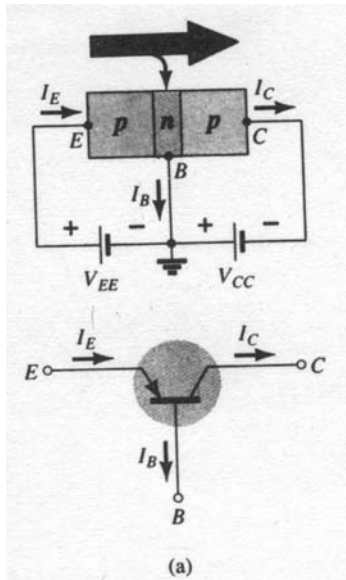 
# BJT



Common base



Common emitter

 

Common collector

Common emitter has a good voltage gain

Common base, good voltage gain, disadvantage of low input impedance

Common collector, voltage gain  $\sim 1$ , high input impedance and low output impedance. Good for impedance matching

# Unipolar Junction Transistors

Unipolar device solely depends on electron ( $n$ -channel) or hole ( $p$ -channel) conduction. Three terminal device.

Field Effect Transistor (FET) is a Unipolar device

Conduction is controlled by the electric field. No need of direct contact between the controlling and controlled quantities

JFET - Junction Field Effect Transistor

MOSFET - Metal Oxide Semiconductor FET


# Junction Field Effect Transistors - JFET

Major part is  $n$ -type material channel, embedded between two  $p$ -type material.

Two ends of the  $n$ - type material channel are Drain (D) and source (S)

Two  $p$ -type material are connected together and referred as Gate (G)

 Two  $pn$  junctions, depletion region at each junction



# Junction Field Effect Transistors - JFET

$V_{GS} = 0$  v and  $V_{DS}$  some positive value


Gate and Source are same potential

Electrons will flow from source to drain as in  $n$  type semiconductor

$$I_D = I_S$$

Resistance of  $n$ -channel acts between drain and source

 
Depletion region is wider near the top of  $p$ -region


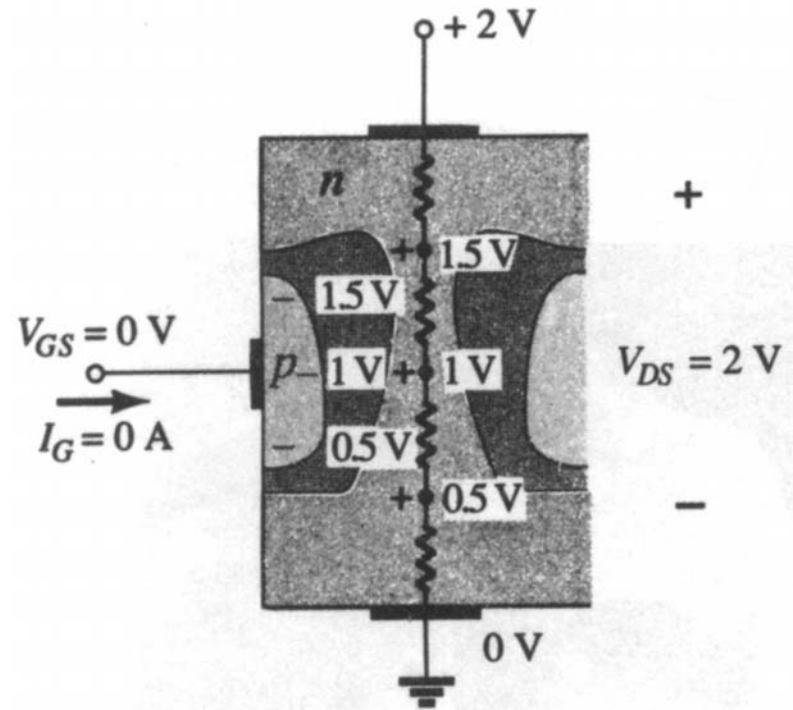
# Junction Field Effect Transistors - JFET

Resistance of  $n$ -channel is uniform along the length. This works as a potential divider.

This leads to a variable reverse bias along the length. Maximum at top of  $p$ -material Reverse bias will depend on the current in  $n$ -channel. More the current more the potential drop







# Junction Field Effect Transistors - JFET

Initially it follows Ohm's law (almost straight line)

Later depletion layer widens

Pinch off level - depletion layer cannot increase more (very high resistance)

  Give a feeling  $I_D$  will be zero. This is not possible




# Junction Field Effect Transistors - JFET

$V_{GS} < 0$  v and  $V_{DS}$  some positive value

Gate to source voltage non zero

 $V_{GS} < 0$  v more reverse bias and hence reduces saturation level for  $I_D$ . This will further reduce with reduction in  $V_{GS}$




# Junction Field Effect Transistors - JFET

Level of  $V_{GS}$  when  $I_D = 0$  is defined as  $V_P$

$V_P$  is negative for  $n$ -channel and positive for  $p$ - channel

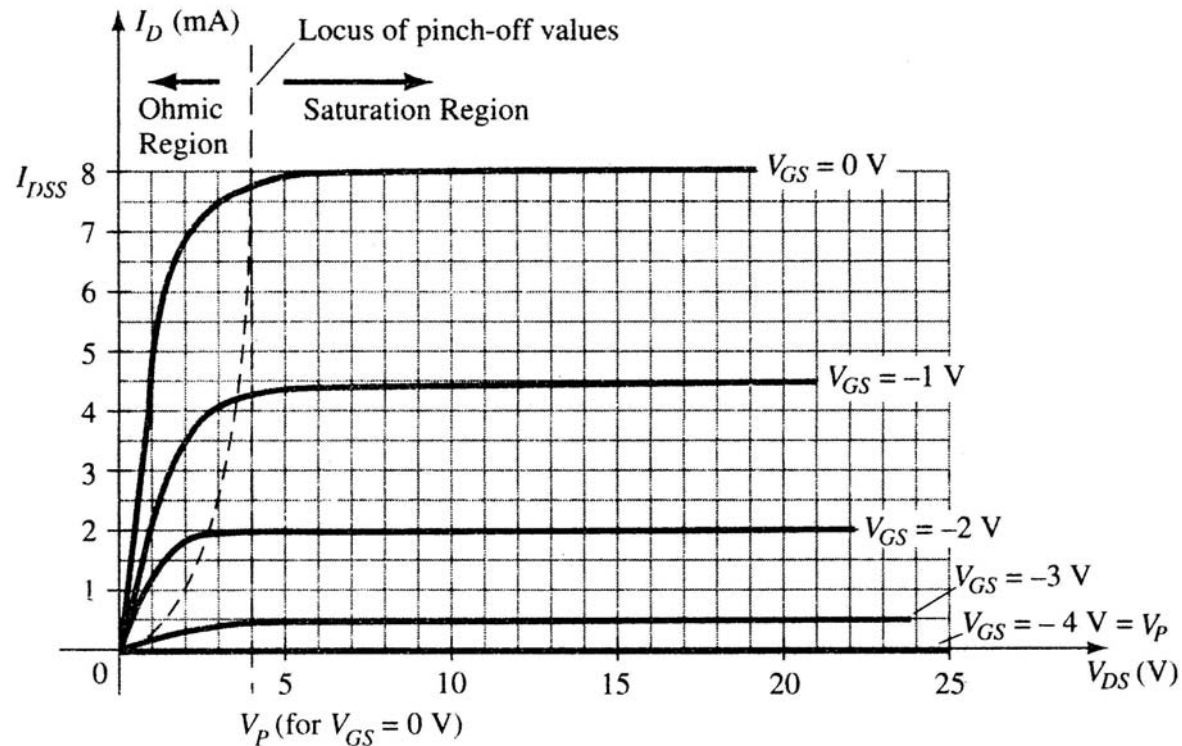
Region left of locus of pinch off values is called as ohmic or voltage controlled resistance ( $V_{DS}$ ). Possible use in automatic gain control, where resistance can be controlled by voltage.


 
# Junction Field Effect Transistors - JFET

*p*-channel type

Behaves exactly same as *n*-channel type. Current direction and the polarities for  $V_{GS}$  and  $V_{DS}$  changes.  $V_{GS}$  is positive and this will create more reverse bias.




# Junction Field Effect Transistors - JFET

*p*-channel type, characteristics

$$V_P > 0$$

 Current is unbounded in the breakdown region. This will damage the transistor.




# Metal Oxide Semiconductor Field Effect Transistors - MOSFET

$n$ -type channel is constructed over a  $p$ -type substrate in form of slab

Many times substrate and source are connected internally and it is a three terminal device

Source and drain are connected at each end of  $n$ -channel

 Gate and  $n$ -channel are separated by insulator  $\text{SiO}_2$  layer (dielectric)




# Depletion type MOSFET-Basic operation

$$V_{GS} = 0\text{V}, V_{DS} > 0$$

Operation similar to JFET


 
Current flows through  $n$ -channel. Free electrons are attracted to positive terminal of drain. Channel ohmic resistance is offered.


  
# Depletion type MOSFET-Basic operation

When  $V_{GS}$  is negative, the electric field will pressure electrons towards  $p$ -type substrate, hence reduce free carrier in  $n$ -channel or depleting the majority carrier

When  $V_{GS}$  is positive it enhances the current. It is limited by the maximum current capacity of the device



Drain and transfer characteristics for an n-channel depletion-type MOSFET.




# Enhancement type MOSFET

$p$ -type substrate in form of slab  
with no  $n$ -channel

Many times substrate and source  
are connected internally and it is  
a three terminal device

Source and drain are connected  
to two  $n$ -doped region

 Gate and  $p$ -substrate are  
separated by insulator  $\text{SiO}_2$  layer  
(dielectric)




# Enhancement type MOSFET

When  $V_{GS} = 0$  and  $V_{DS} > 0$

No link between two  $n$ -doped region and hence no current

 
$V_{GS}$  and  $V_{DS} > 0$  This will push the holes away from the  $\text{SiO}_2$  edge and attracts electrons from the  $p$ -substrate. When sufficient voltage is applied it creates a  $n$ -channel, this is called threshold voltage  $V_T$


 
# Enhancement type MOSFET

If  $V_{GS}$  is increased beyond threshold voltage,  $I_D$  will increase.


If  $V_{GS}$  is kept constant beyond threshold voltage, and  $V_{DS}$  is increased then  $I_D$  will reach saturation level similar to JFET (pinch off)



# Enhancement type MOSFET

Values less than threshold value  $I_D$  is zero


$V_{GS}$  increases  $V_{DSsat}$

 

Drain characteristics of an  $n$ -channel enhancement-type MOSFET with  $V_T = 2$  V and  $k = 0.278 \times 10^{-3}$  A/V<sup>2</sup>.

 
# Darlington Pair circuit

Used as high current current component. Current amplification of the order of  $\beta^2$  Can be easily integrated with microcontroller for interfacing DC motor, relays etc.


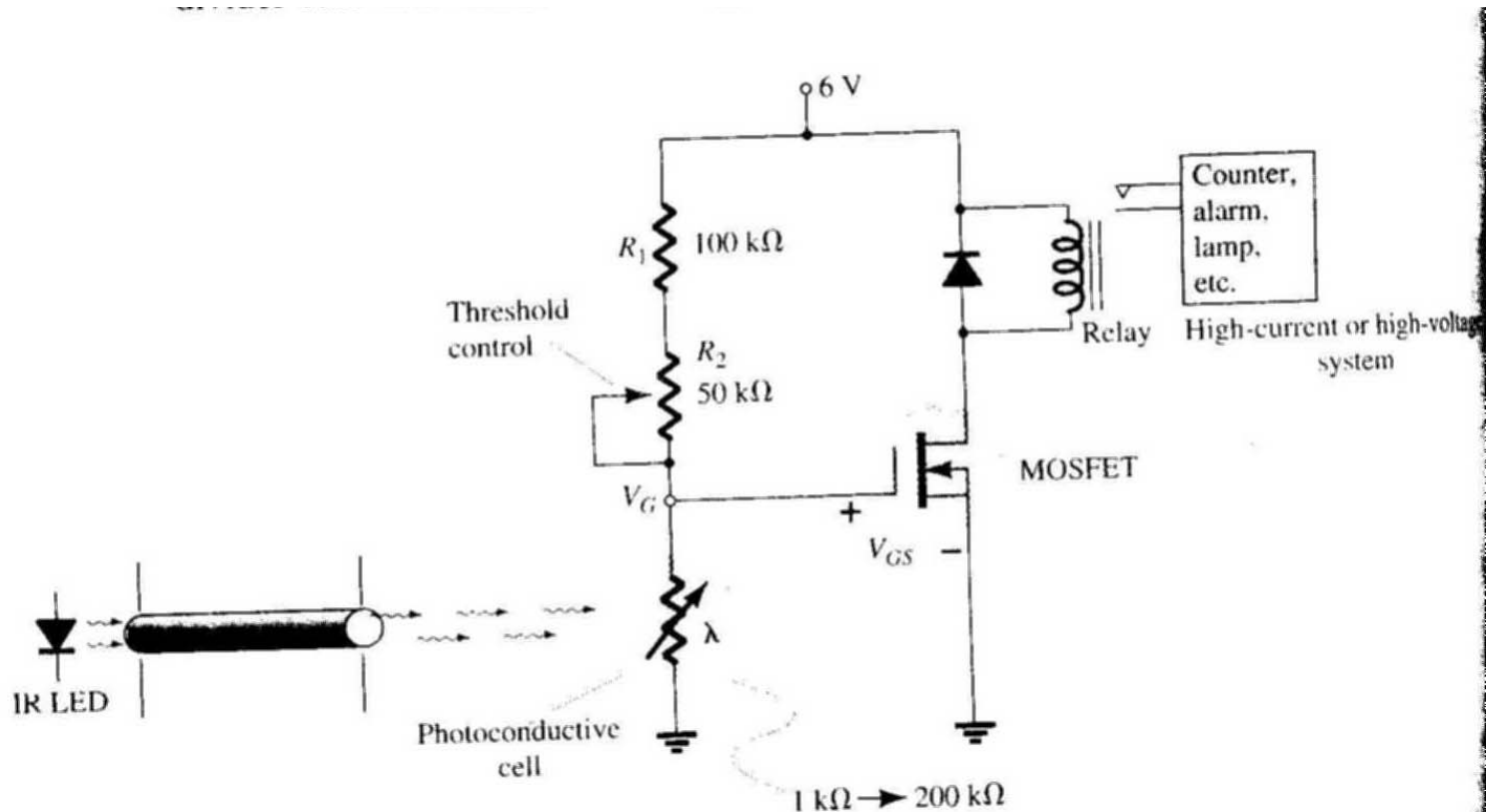
# MOSFET as relay driver

When photodiode not conducting Gate is positive and no current in MOSFET. When photodiode is conducting Gate is grounded and current is passed through MOSFET.



# BJT and UJT



BJT - Current controlled devices

- electron & holes participate in conduction
- Robust in handling

UJT - Voltage controlled devices

- Only one type of carrier participate in conduction
- Smaller in size and more devices can be packed
- Sensitive to static charge (MOSFET)
- Very high input impedance
- Less noisy

# BJT symbols

  


BJT

a) *pnp*

b) *npn*



# UJT symbols








 


*n*-channel

*p*-channel

*n*-channel

*p*-channel

        

(a)

(b)

JFET a) *n*- channel

b) *p*- channel

MOSFET enhancement

a) *n*- channel

b) *p*- channel

MOSFET depletion

a) *n*- channel

b) *p*- channel

